



The University of  
**Nottingham**

UNITED KINGDOM • CHINA • MALAYSIA

DEPARTMENT OF ELECTRICAL AND ELECTRONIC  
ENGINEERING FACULTY OF ENGINEERING

ELECTRONIC PROCESSING AND COMMUNICATIONS

(EEEE2044 UNUK) (FYR1 22-23)

---

# LTspice Simulation of Sequential Circuits

---

Author:  
George Downing

Student Number:  
20273662

October 24, 2022

## Contents

Question 1	2
Question 2	2
Question 3	3
Question 4	4
Question 5	4
Question 6	5
Question 7	5
Question 8	5
Question 9	6
Question 10	6
Question 11	6
Question 12	7
Question 13	8
Question 14	8
Question 15	9
Question 16	10
Question 17	10
Question 18	10
Question 19	10
Question 20	10
References	10

## Question 1

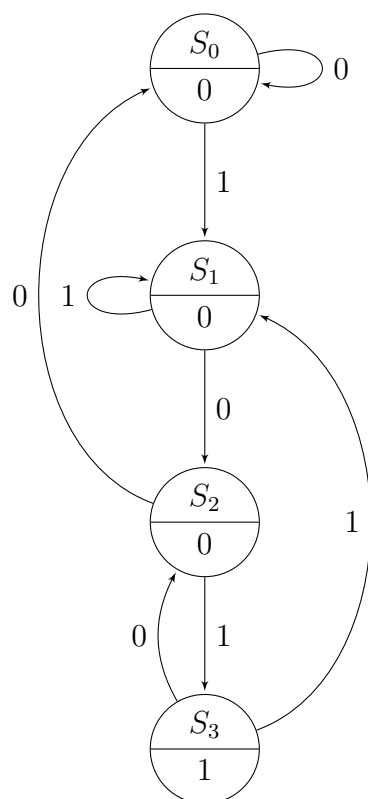


Figure 1: State Diagram for Q1

## Question 2

<i>Present State</i> ( <i>n</i> )	Next State ( <i>n</i> +1)		Present Output <i>Z</i>
	X=0	X=1	
$S_0$	$S_0$	$S_1$	0
$S_1$	$S_2$	$S_2$	0
$S_2$	$S_0$	$S_3$	0
$S_3$	$S_2$	$S_1$	1

Table 1: State Transition Table in terms of  $S_0$  and  $S_1$

<i>Present State (n)</i>		Next State (n+1)				D-inputs required				Output Z
		X = 0		X = 1		X = 0		X = 1		
$Q_n^A$	$Q_n^B$	$Q_{n+1}^A$	$Q_{n+1}^B$	$Q_{n+1}^A$	$Q_{n+1}^B$	$D_A$	$D_B$	$D_A$	$D_B$	
0	0	0	0	0	1	0	0	0	1	0
0	1	1	0	0	1	1	0	0	1	0
1	0	0	0	1	1	0	0	1	1	0
1	1	1	0	0	1	1	0	0	1	1

Table 2: State Transition Table in terms of  $Q_n^A$  and  $Q_n^B$ 

### Question 3

X	$Q_n^A Q_n^B$			
	00	01	11	10
0	0	1	1	0
1	0	0	0	1

Figure 2: Karnaugh map for the Input of flip-flop  $D_A$ 

X	$Q_n^A Q_n^B$			
	00	01	11	10
0	0	0	0	0
1	1	1	1	1

Figure 3: Karnaugh map for the Input of flip-flop  $D_B$ 


$$D_A = Q_n^B \cdot \overline{X} + Q_n^A \cdot \overline{Q_n^B} \cdot X \quad (1)$$

$$D_B = X \quad (2)$$

$$Z = Q_n^A \cdot Q_n^B \quad (3)$$

Eq. 1 is the input of flip-flop  $D_A$  derived from the Karnaugh map as shown in figure 2. Eq. 2 is the input of flip-flop  $D_B$  derived from the Karnaugh map as shown in figure 3. Eq. 3 is the output of the flip-flop  $D_A$  as shown by Table 2.

## Question 4

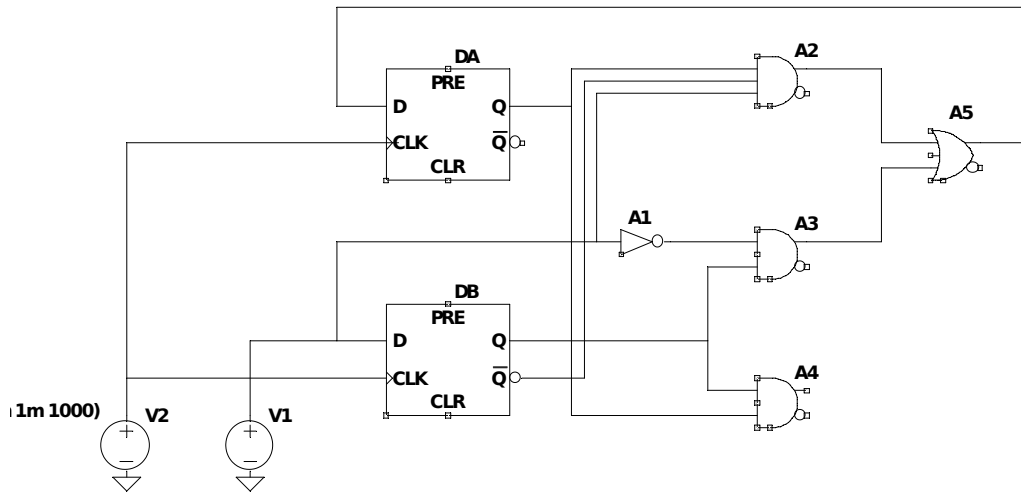

## Question 5

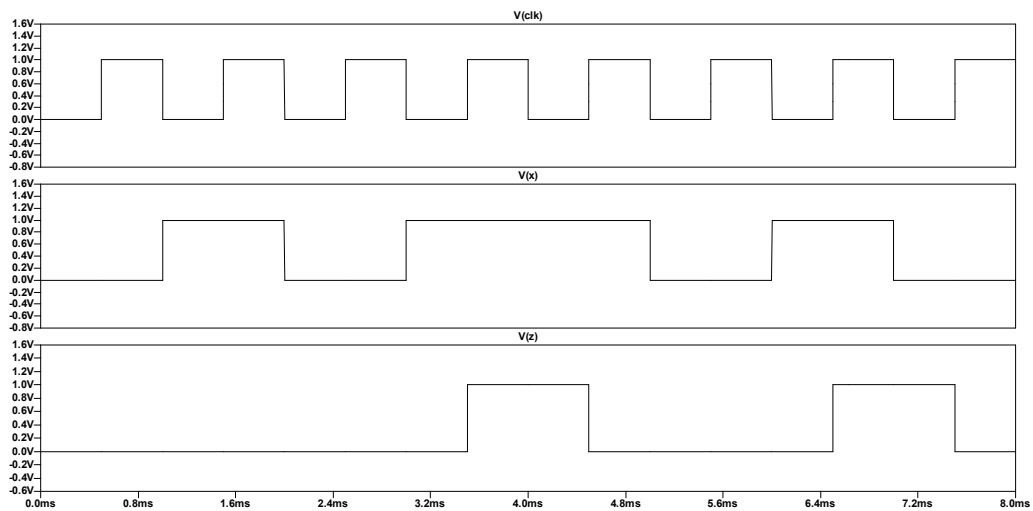


Figure 4: LTspice Simulation Traces V(CLK), V(X) and V(Z) for Q5

## Question 6

$$t_{AFGCD} = t_{pd} + t_{A1} + t_{A5} \quad (4)$$

$$t_{DGCD} = t_{pd} + t_{A1} + t_{A5} \quad (5)$$

Eq. 4 and 5 denote the delay through paths  $t_{DGCD}$  and  $t_{AFGCD}$ .

## Question 7

$$t_{JGCD} = t_{A1} + t_{A5} \quad (6)$$

Eq. 6 denotes the delay through path  $t_{JGCD}$ .

## Question 8

$$\begin{aligned} t_{AEBCD} &= t_{pd} + t_{A2} + t_{A5} \\ &= 40ns + 27ns + 22ns \\ &= 89ns \end{aligned} \quad (7)$$

$$\begin{aligned} t_{AFGCD} &= t_{pd} + t_{A1} + t_{A5} \\ &= 40ns + 27ns + 22ns \\ &= 89ns \end{aligned} \quad (8)$$

$$\begin{aligned} t_{DGCD} &= t_{pd} + t_{A1} + t_{A5} \\ &= 40ns + 27ns + 22ns \\ &= 89ns \end{aligned} \quad (9)$$

Eq. 7, 8 and 9 denote the delay through paths  $t_{AEBCD}$ ,  $t_{AFGCD}$  and  $t_{DGCD}$  respectively. The maximum delay of these three paths is  $t_{min} = 89ns$ .

## Question 9

$$\begin{aligned}
 t_{JHBCD} &= t_{A4} + t_{A2} + t_{A5} \\
 &= 22ns + 27ns + 22ns \\
 &= 71ns
 \end{aligned} \tag{10}$$

$$\begin{aligned}
 t_{JGCD} &= t_{A1} + t_{A5} \\
 &= 27ns + 22ns \\
 &= 49ns
 \end{aligned} \tag{11}$$

Eq. 10 and 11 denote the delay through paths  $t_{JHBCD}$  and  $t_{JGCD}$  respectively. the maximum delay of these two paths is  $t_{min} = 71ns$ .

## Question 10

 


Figure 5: LTspice Simulation Traces V(CLK), V(X) and V(Z) for Q10

## Question 11

 


Figure 6: LTspice Simulation Traces V(CLK), V(X) and V(Z) for Q11

Figure 7 shows the output V(Z) as a flat line indicating the circuit is not operating correctly due to being clocked too fast.

V(X) is clocked on the falling edge of V(CLK) and V(Z) is clocked on the rising edge of V(CLK). This means any change in V(X) only has half a clock cycle to propagate to the input of  $D_a$ .  $t_{JHBCD} = 71ns$  which is more than half of the clock cycle (60ns) when  $t_{CLK} = 120ns$ . This means the circuit is not operating correctly due to being clocked too fast.

## Question 12



 


Figure 7: LTspice Simulation Traces V(CLK), V(X) and V(Z) for Q12

Figure 7 shows the output V(Z) now producing the correct output when clocked at 120ns. Introducing a delay of 10ns, the time between a change in V(x) and the rising edge of V(CLK) now becomes  $60ns + 10ns + 0.5ns = 70.5ns$ , where the 10ns is the additional delay and 0.5ns, the delay caused by a 1ns rise time. the measured value of  $t_{JHBCD} = 70.36$  which is less than 70.50ns therefore will propagate in time V(Z) to be clocked.

## Question 13

State	Description of state
$S_0$	Initial State/Last bit is '0'
$S_1$	Detect '1' in most recent bit.
$S_2$	Detect '10' in most recent two bit.
$S_3$	Detect '100' in most recent two bit.
$S_4$	Detect '1000' in most recent two bit.

Table 3: State description table for mealy machine to detect the sequence 10001

## Question 14

ID	20273662
Test sequence	10001
Test stream	11111100011001110100011110

Table 4: Data for Q14

 


Figure 8: State Diagram for Q14

## Question 15

The number of flip flops required is  $\lceil \sqrt{n} \rceil$  where  $n$  is the number of states. In this case,  $n = 5$  so  $\lceil \sqrt{5} \rceil = 3$  flip flops are required. The flip-flop state allocation is shown in table 5 below.

State	Flip Flop Output		
	$Q^A$	$Q^B$	$Q^C$
$S_0$	0	0	0
$S_1$	0	0	1
$S_2$	0	1	0
$S_3$	0	1	1
$S_4$	1	0	0

Table 5: Flip Flop State Allocation

**Question 16****Question 17****Question 18****Question 19****Question 20****References**