The University of Nottingham

UNITED KINGDOM · CHINA · MALAYSIA

Department of Electrical and Electronic Engineering Faculty of Engineering

Practical Engineering Design Solutions and Project Development

(EEEE2046 UNUK) (FYR1 22-23)

Filter Design Coursework

Author:
George Downing

Student Number:
20273662

October 24, 2022

Contents

1 Introduction **2**
1.1 Background . . . 2
1.2 Butterworth Filter . . . 2
1.3 Chebyshev Filter . . . 2
1.4 Multiple Feedback Filter Topology . . . 2

2 Results **2**
2.1 Design requirements and specification . . . 2
2.2 Calculations . . . 2
2.3 Simulation Results . . . 2
2.4 Schematic Design in LTSpice . . . 2

3 Discussion **2**
3.1 Calculations for E24 Series Components . . . 2
3.2 Schematic Design for E24 Series Components . . . 2
3.3 Results of Changing to E24 Series Components . . . 2
3.4 Effect of Component Tolerances . . . 2
3.5 Design to Include Additional Amplification . . . 2

4 Conclusion **2**

References **2**

Appendices **2**
A Matlab Code . . . 2
B LTSpice Code . . . 2

1 Introduction

1.1 Background

1.2 Butterworth Filter

1.3 Chebyshev Filter

1.4 Multiple Feedback Filter Topology

2 Results

2.1 Design requirements and specification

2.2 Calculations

2.3 Simulation Results

2.4 Schematic Design in LTSpice

3 Discussion

3.1 Calculations for E24 Series Components

3.2 Schematic Design for E24 Series Components

3.3 Results of Changing to E24 Series Components

3.4 Effect of Component Tolerances

3.5 Design to Include Additional Amplification

4 Conclusion

References

Appendices

A Matlab Code

B LTSpice Code