



University of
Nottingham

UK | CHINA | MALAYSIA

A large, detailed image of the Earth as seen from space, showing the Western Hemisphere with North and South America. The Earth is framed by a thin white rectangular border. The background is a dark, starry space.

Individual Filter Design Coursework -Electronic Project-

Dr. Ahmed Aldabbagh

Dr. Ricardo Correia

Dr. Dan Fallows



Filter Design Coursework EEEE2046

Introduction



Learning outcomes

- Enhance the level of understanding in filter design specifically higher order filter.
- Appreciate issues in designing filter using different approaches
- Improve learner skills in designing course work document.





Aim

- The aim of this individual coursework is to design a higher order filter that can better attenuate the low frequency components, i.e. a **high pass filter**




Electronic Project EEEE2046

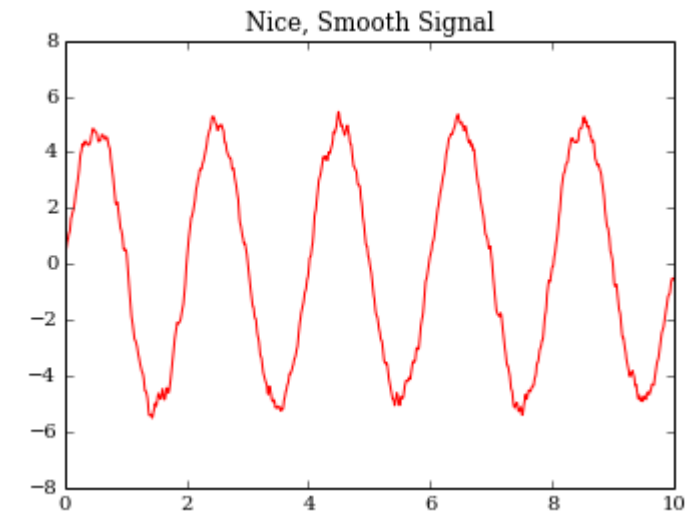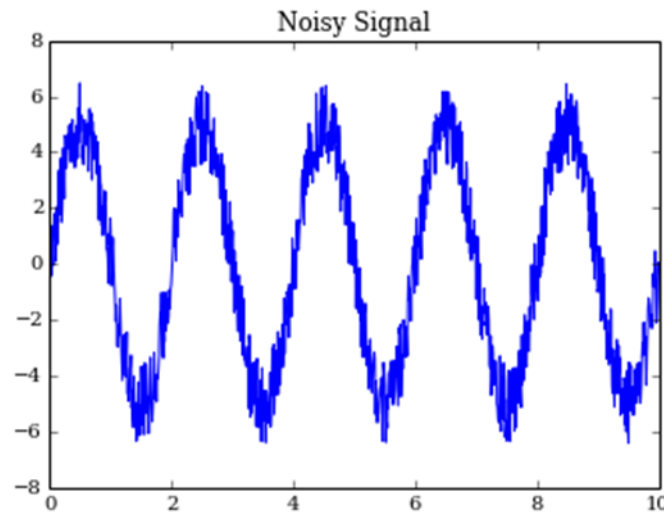- Theoretical material on filters is covered in EEEE2044: Electronic Processing and Communications module / filter section.
- Why do we filter?
- Filter are used in most of the area of Electrical and Electronic Engineering
- The signals usually corrupted with noise
- We are aiming to reduce the effect of these noises ... but to perfect level





Electronic Project EEEE2046

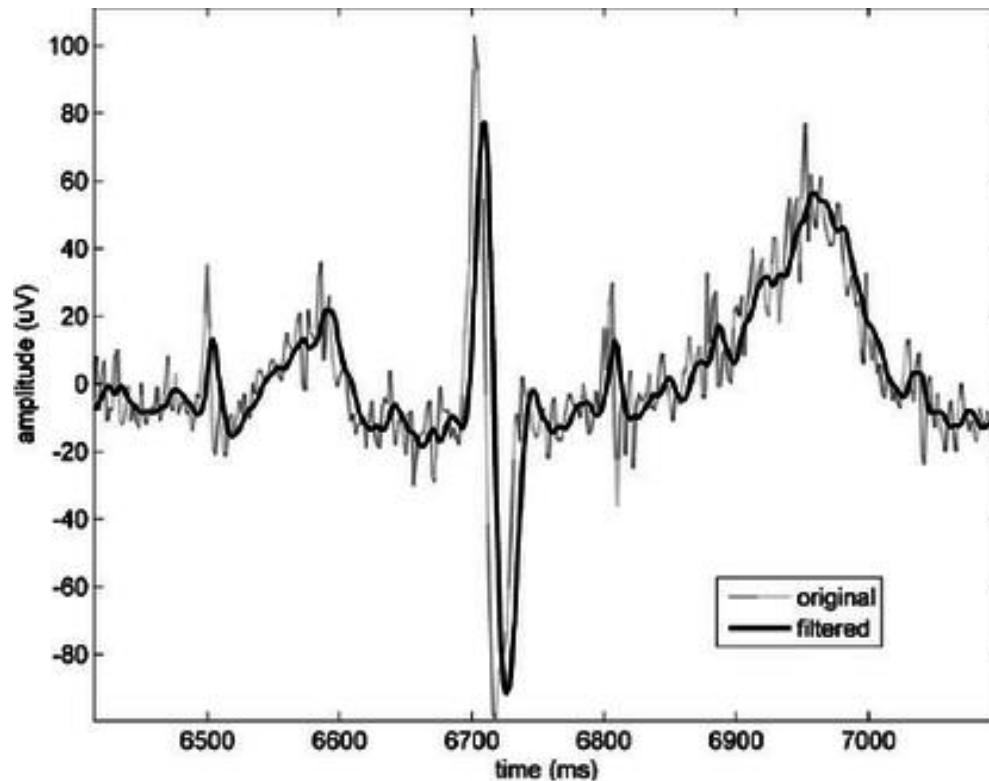

e.g. Biomedical signal

- Filtered signal is much smoother
- Don't over filter the signal and remove important information

R E Gregg, S Zhou, J Lindauer and E Helfenbein, Journal of Electrocardiography, 41(1),8-14, February 2008




Electronic Project EEEE2046

Key filter functions are:

Amplitude response : dependent on frequency, important to decide the type of your filter H or L pass.

Phase response

- Phase response

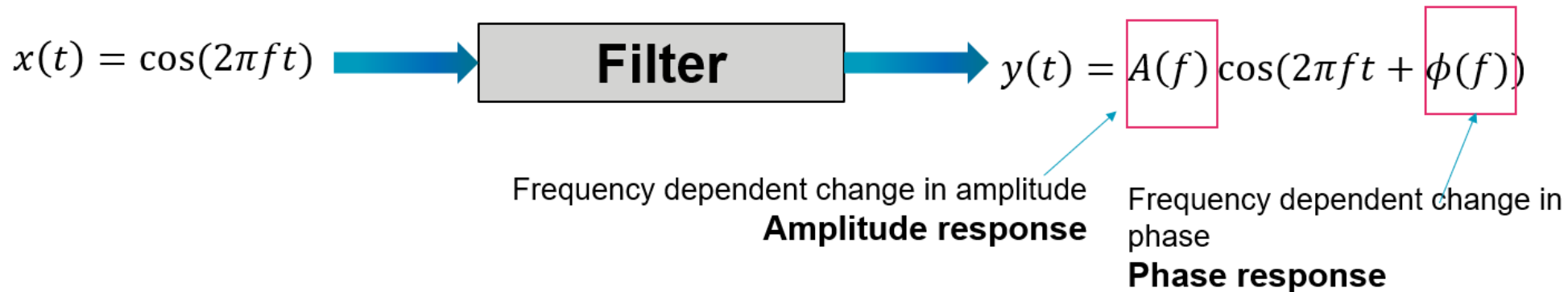



Electronic Project EEEE2046



Doppler Frequency Proportional to Speed

$$f_0 \longrightarrow f_0 + f_d \propto V$$

Doppler returns from cars with speeds between V_{min} and V_{max}


Doppler frequencies between f_d^{min} and f_d^{max}

But also returns from grass bank, trees, birds, - clutter !!!

Also wideband noise affecting instrumentation




Electronic Project EEEE2046

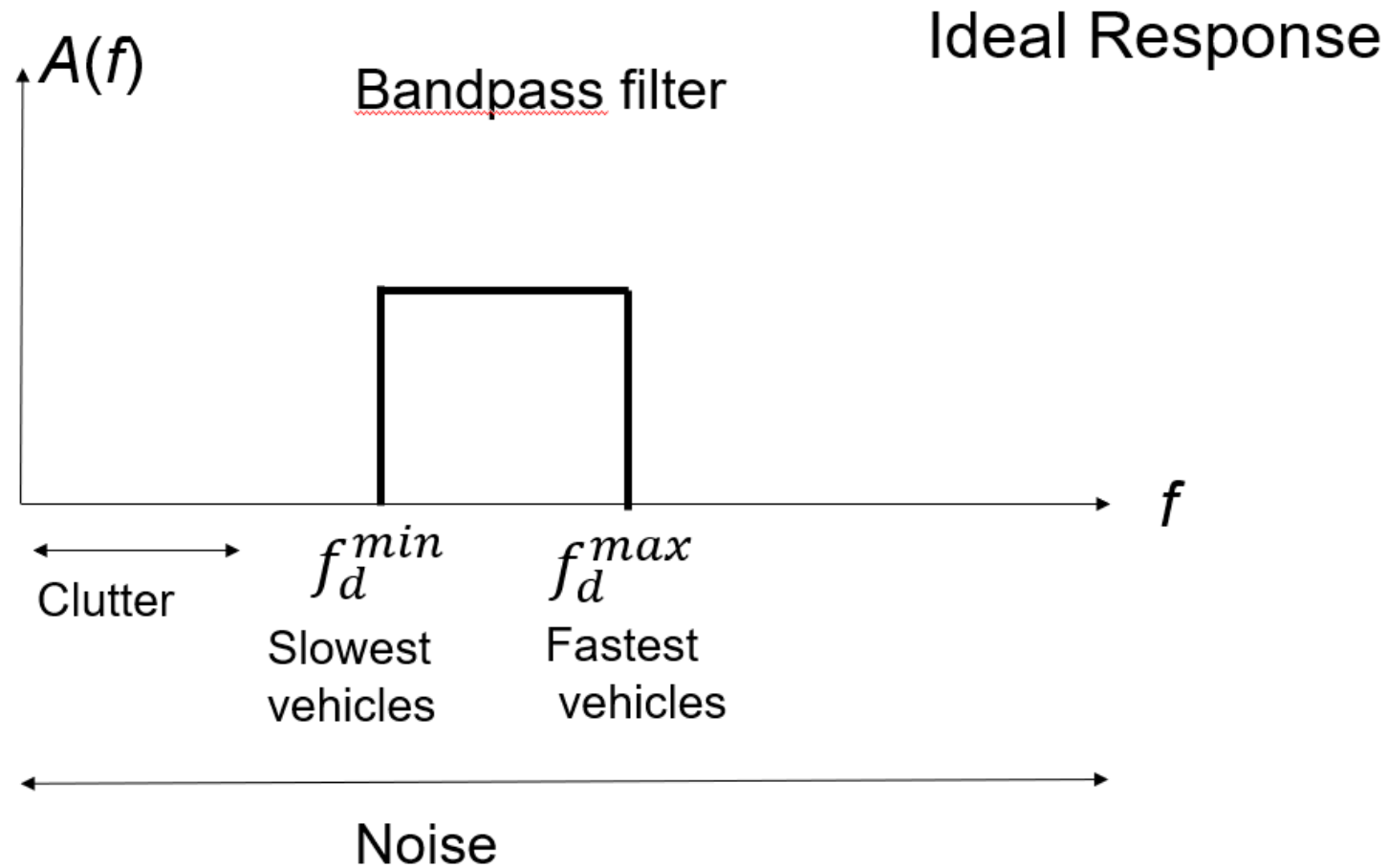




Electronic Project EEEE2046

Filter types

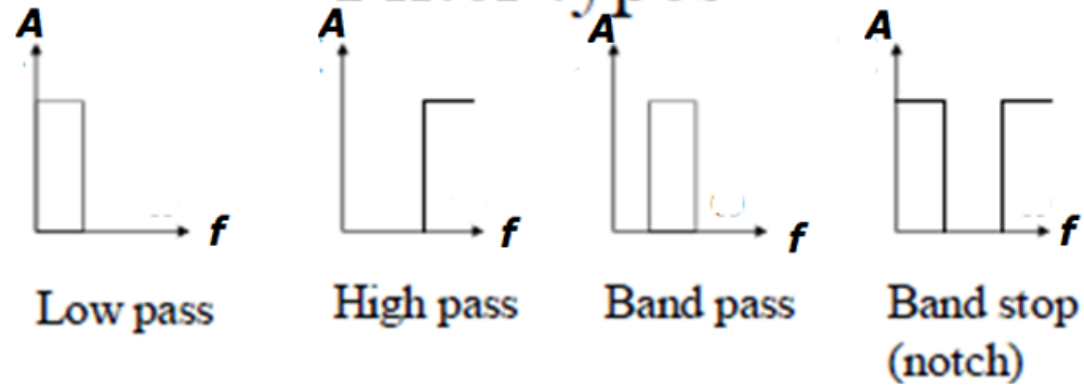

In
practice.....

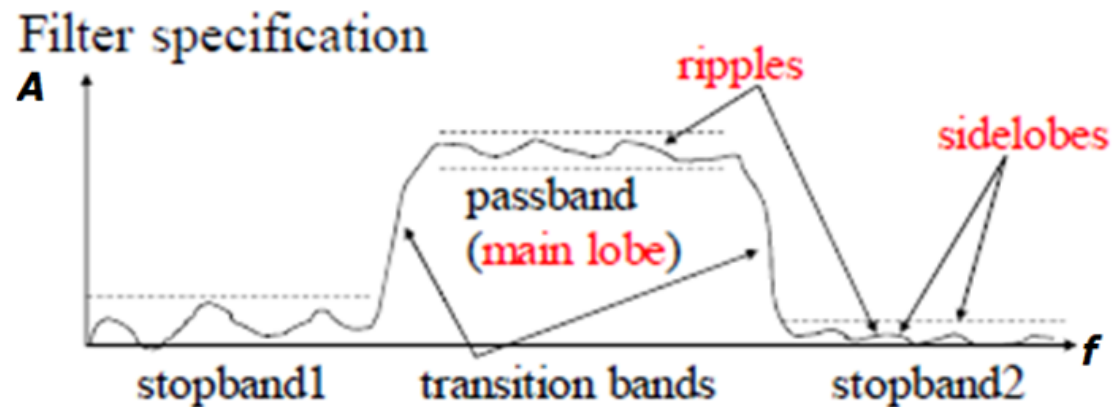



Electronic Project EEEE2046

Tasks 1 & 2:


- Analogue signal conditioning -> gain and filter

Your group have designed filters for your Doppler radar system.

As you may have seen with your experimental results – these filters are less than ideal.

The purpose of the filter design coursework is to:

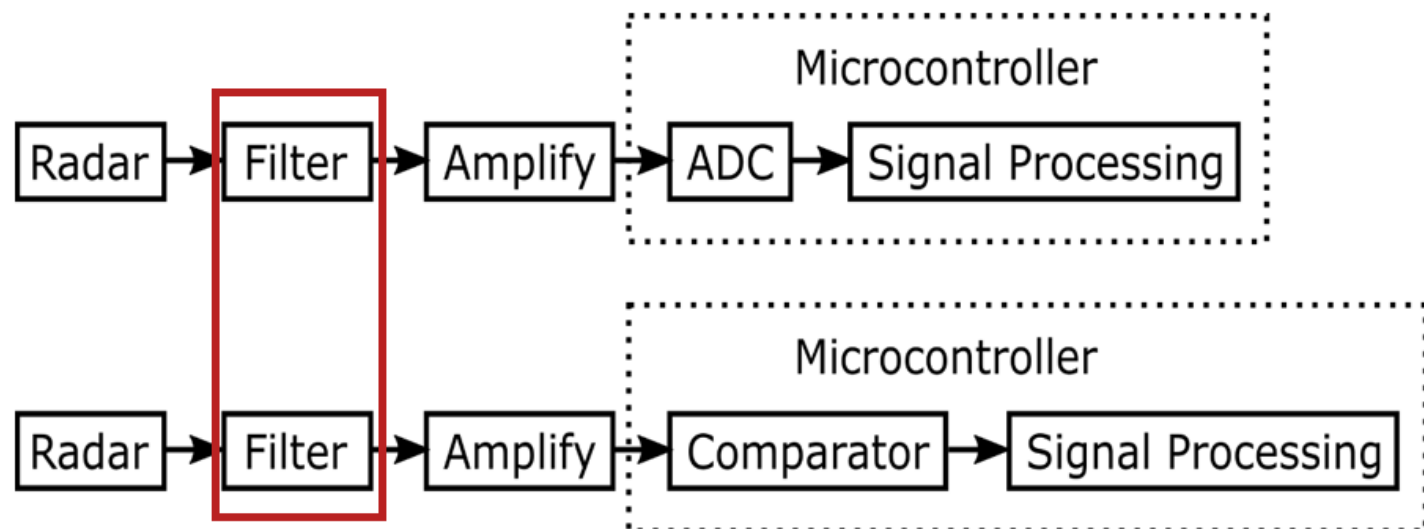
- Build upon your experiences in the laboratory to consider an improved system.
- Apply and link theoretical work you've done in EEEE2044: Electronic Processing and Communications with the experimental work in your project.





Electronic Project EEEE2046

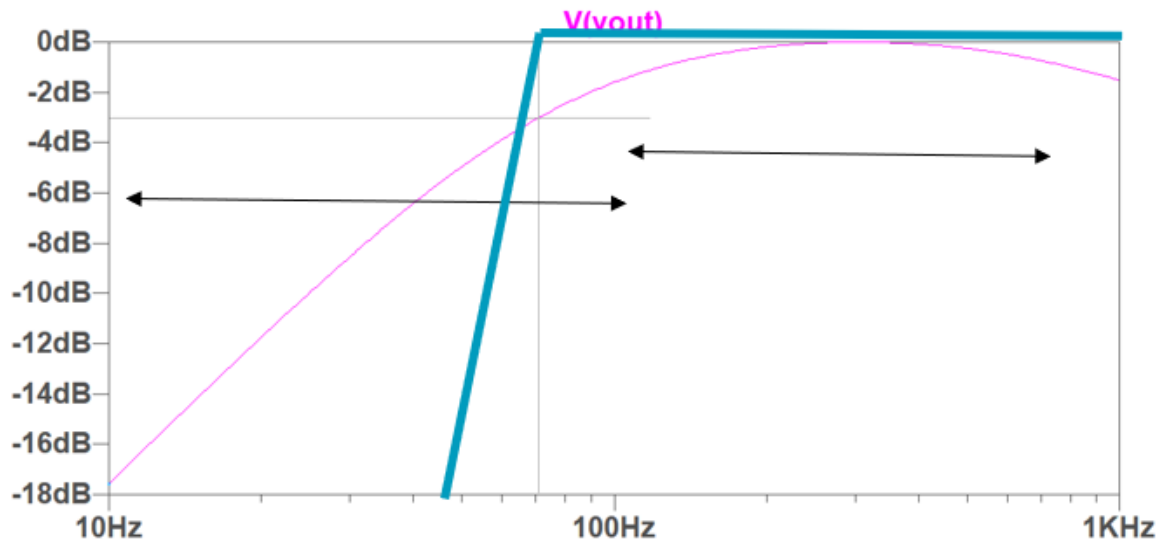So far, you have designed a filter with the following response




Non-ideal response because:

- Not a flat response in the passband
- Some unwanted frequencies passed by the filter

The aim of this coursework is to make the low frequency response sharper – high pass filter



Electronic Project EEEE2046

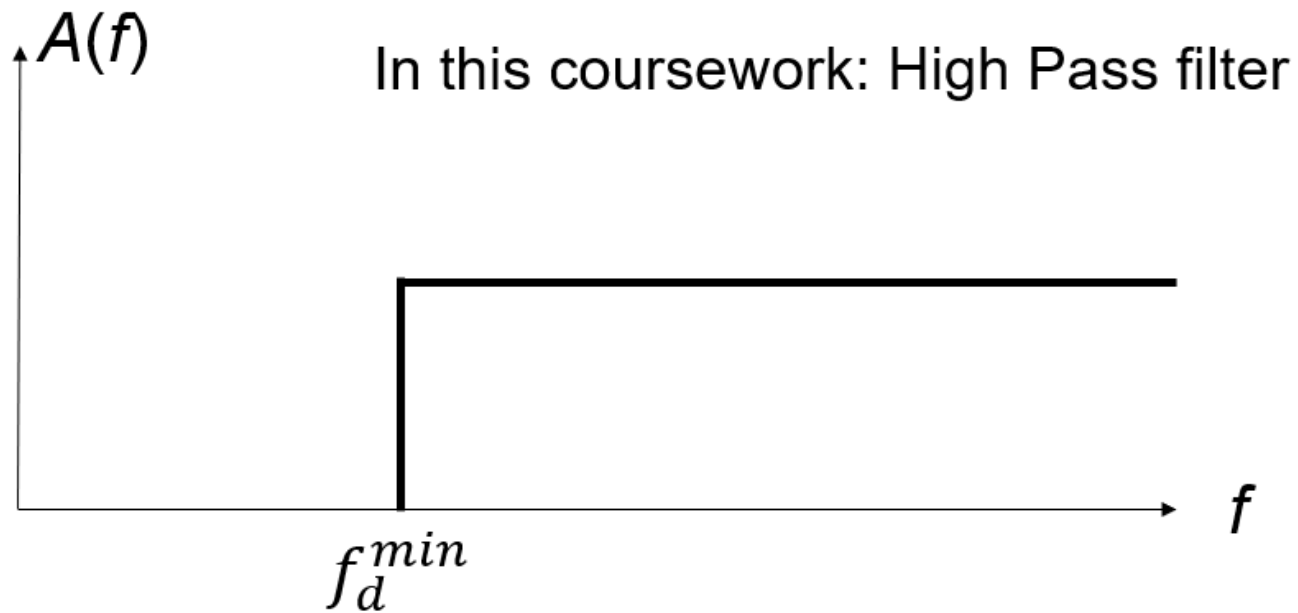


Again this response is ideal




Electronic Project EEEE2046

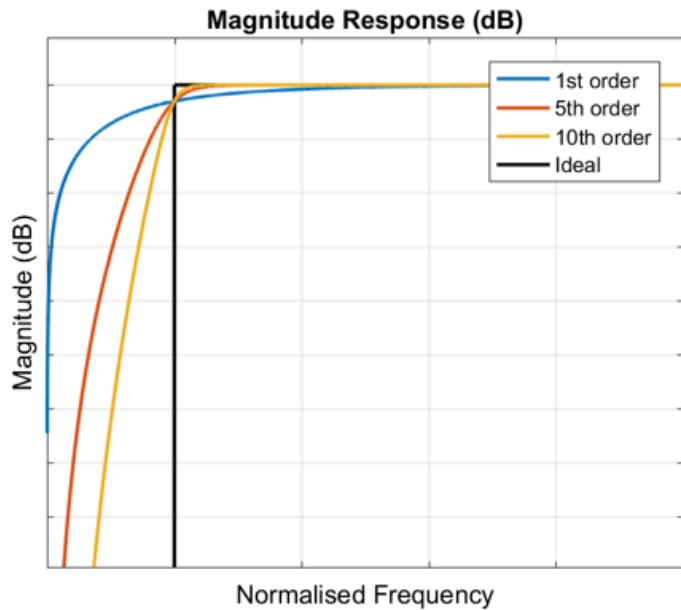The more components, the sharper the response




e.g. Third Order = Cascade First Order followed by Second Order

Second Order: Sallen key filter

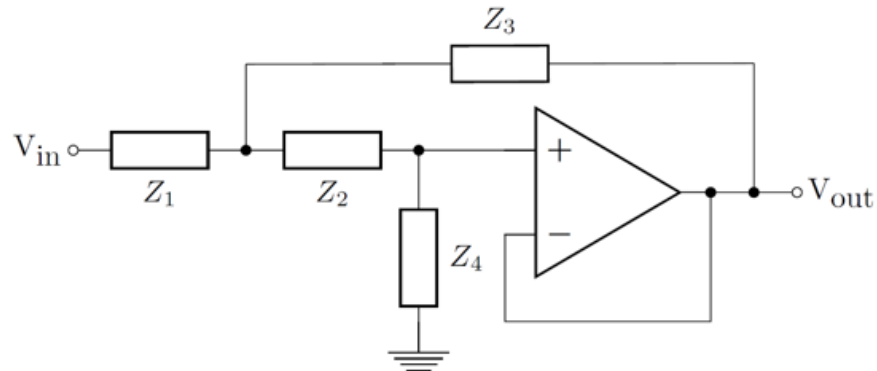


First Order Section

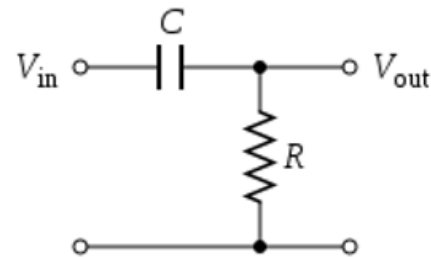



Electronic Project EEEE2046

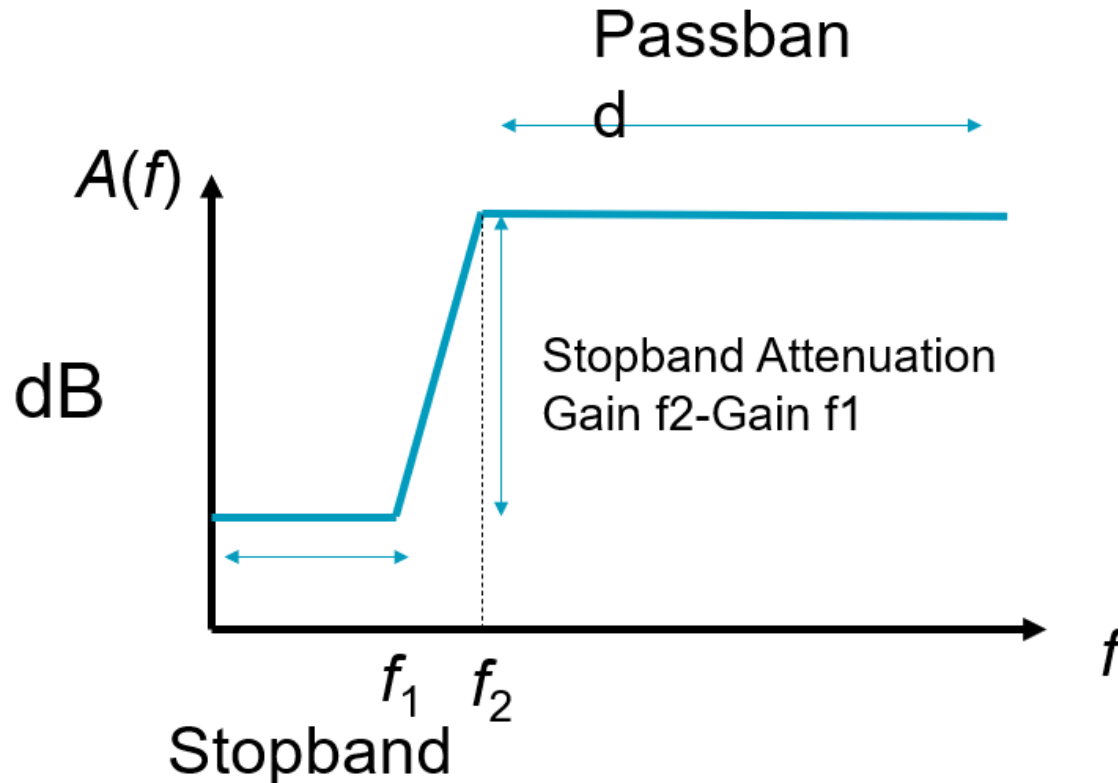

The steeper the transition between Passband and Stopband, the higher the order of the filter
 f_1 : end of the stop band
 f_2 : frequency corresponding to beginning of pass band : 3dB freq

Need to use a minimum order satisfying design specification to avoid using unnecessarily large number of components



Electronic Project EEEE2046

The coursework task will lead you through a number of design steps and ask you to write up your findings.

In EEEE2044, we will be discussing filters in more detail and provide you with a more comprehensive overview of filter design.

If, after completing the coursework you think your filters in the project can be improved, I recommend that you do not change your circuit at this late point (unless you are having major issues with your signal input to the microcontroller) and instead be prepared to discuss improvements in your viva.



Submission

- [illegible]



Page limit

- Absolute maximum of 10 pages (including all tables, charts, references etc.) Cover page not included.
- Anything over the page limit will not be read/marked
- Marking Rubric : Coursework Assessment Criteria

<https://moodle.nottingham.ac.uk/mod/resource/view.php?id=5926784>



Report structure

- 1- Introduction: background, filter types, advantages, and disadvantages..
- 2- Filter circuit design calculations and description.
- 3- Results: Simulation results
- 4- Discussion
- 5- Conclusion (optional)
- 6- References
- 7- Appendix (optional).



Report structure

IMPORTANT

- No screenshots for calculations/ no mobile photos
- No handwriting in your report / including using ipad or any similar devices.
- For equations: use word (or any other software) → insert symbols → equation → insert new equation.
- For tables: use word (or any other software) → insert table → or draw table
- No results figures or calculations in Appendix



Task 1

- Carry out research into different filter characteristics and their applications. Provide a description of the advantages and disadvantages of each of Butterworth, Chebyshev and Bessel filter designs and include examples of where these filters can be found in real life products.
- No Wikipedia references
- Use IEEE numbering as a reference style



Task 2

- Design and simulate a high pass Butterworth filter using the Sallen Key topology, to meet the following specification:
- Gain: 1
- Pass band: $100 + (\text{use your student ID last 2 digits}) \text{ Hz}$
- Stop band: 50Hz
- Stop band attenuation: 30dB




Task 3

- Create a new copy of your design that uses resistor and capacitor values that are readily available. Resistor and capacitor values are typically available in so-called “E” ranges.




Good design- example

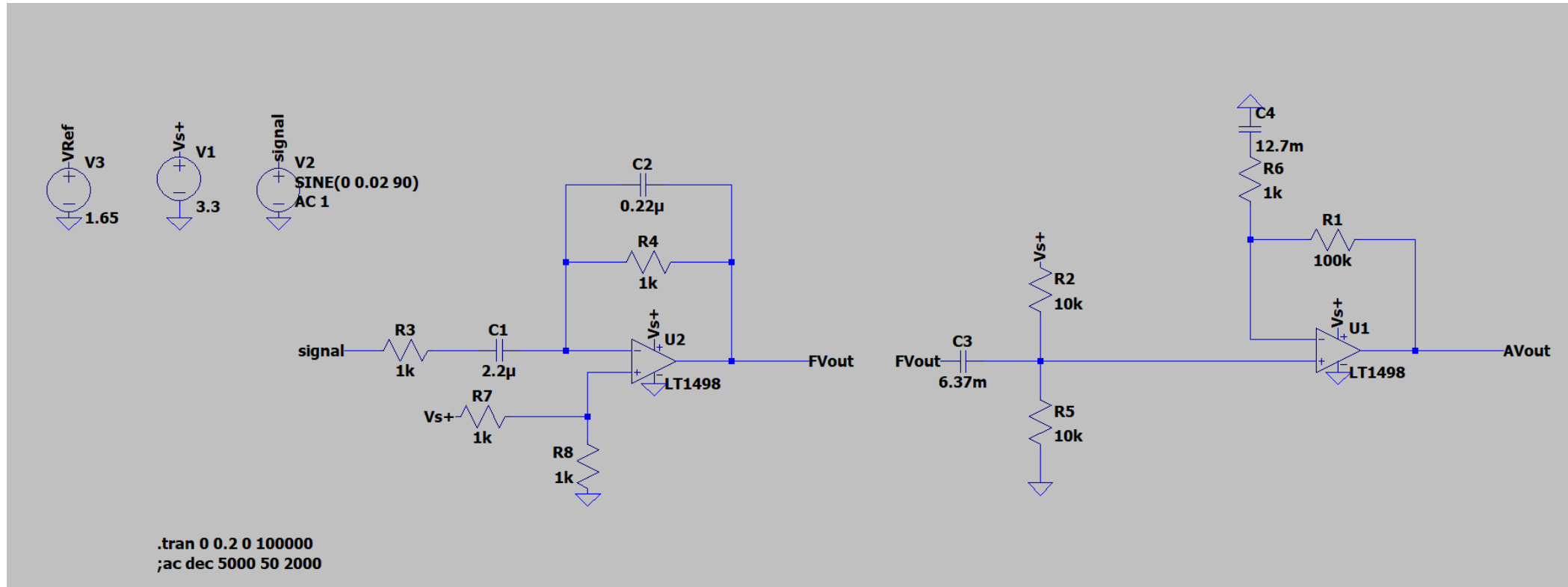



Poor design- example

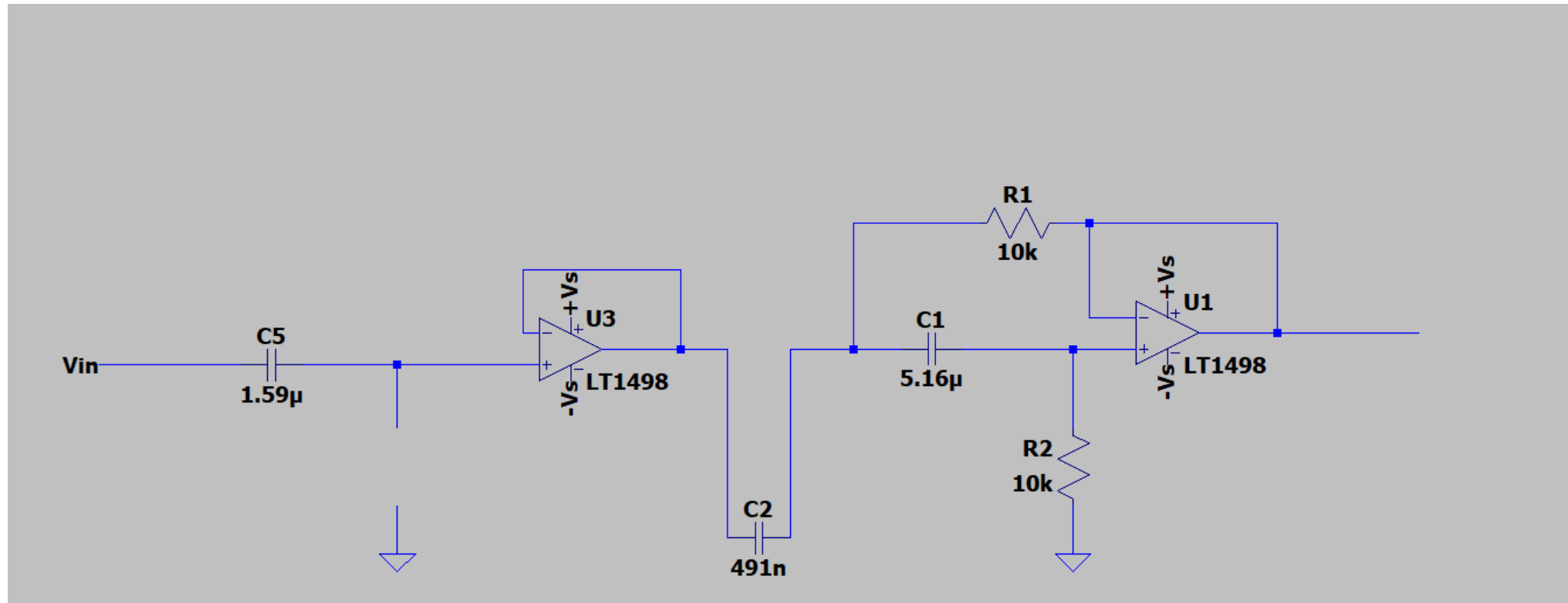



University of
Nottingham

UK | CHINA | MALAYSIA

Thank you